

Computer Science CSCI 355

Digital Logic and Computer Organization

Dr. Peter Walsh

Department of Computer Science

Vancouver Island University

peter.walsh@viu.ca

Logic Families

A logic family refers to a set of techniques used to implement logic within an integrated circuit.

- Transistor Transistor Logic (TTL)
 - circuits use bipolar junction transistors (BJT)
- Complementary-Symmetry Metal-Oxide-Semiconductor (CMOS)
 - circuits use field effect transistors (FET)

CMOS Logic

Complementary-Symmetry Metal-Oxide-Semiconductor is a type of metal-oxide semiconductor field-effect transistor fabrication process that uses complementary and symmetrical pairs of p-type and n-type transistors for logic functions (see CMOS Wikipedia entry).


- Advantages (over TTL)

- lower power consumption
- reduced complexity
- higher packing density
- better noise tolerance
- better fan-in and fan-out capabilities

- Disadvantages (over TTL)


- susceptible to electrostatic discharge
- higher propagation delay

CMOS Circuits

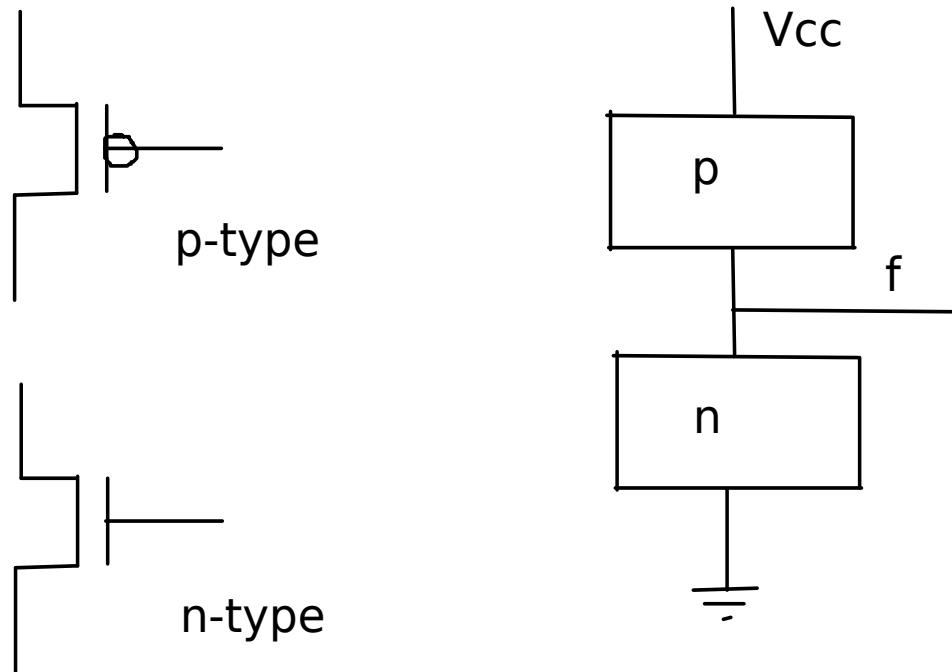


CMOS Circuits cont.

- Complementary

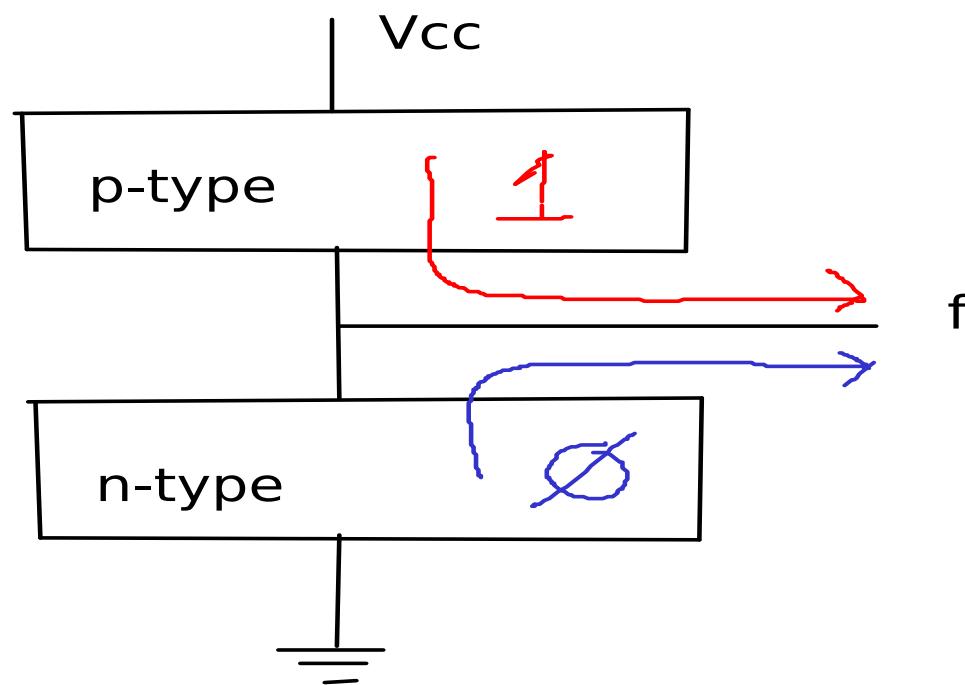


CMOS Circuits cont.


- Symmetry

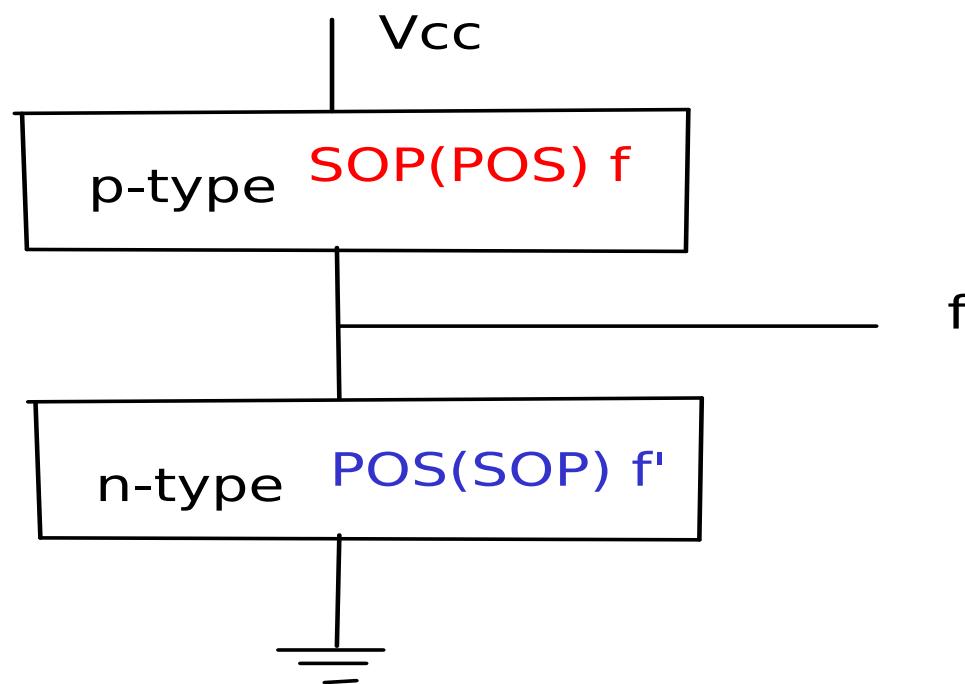


CMOS Inverter Gate

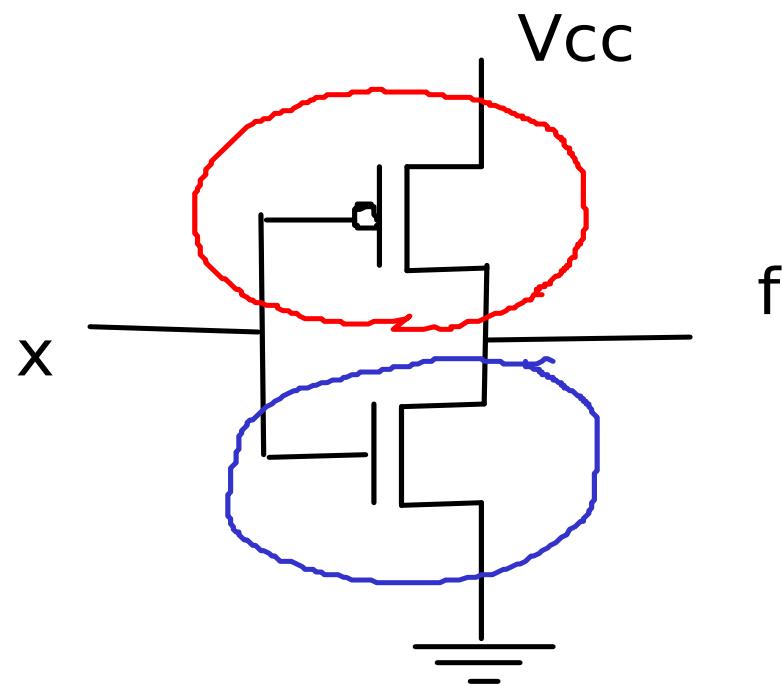


CMOS Nor Gate

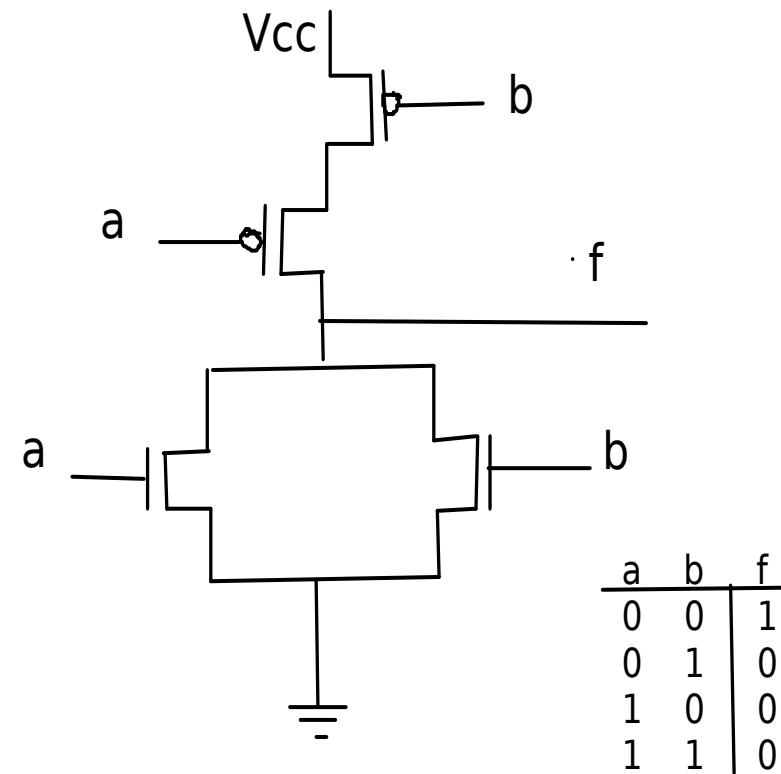


CMOS Or Gate

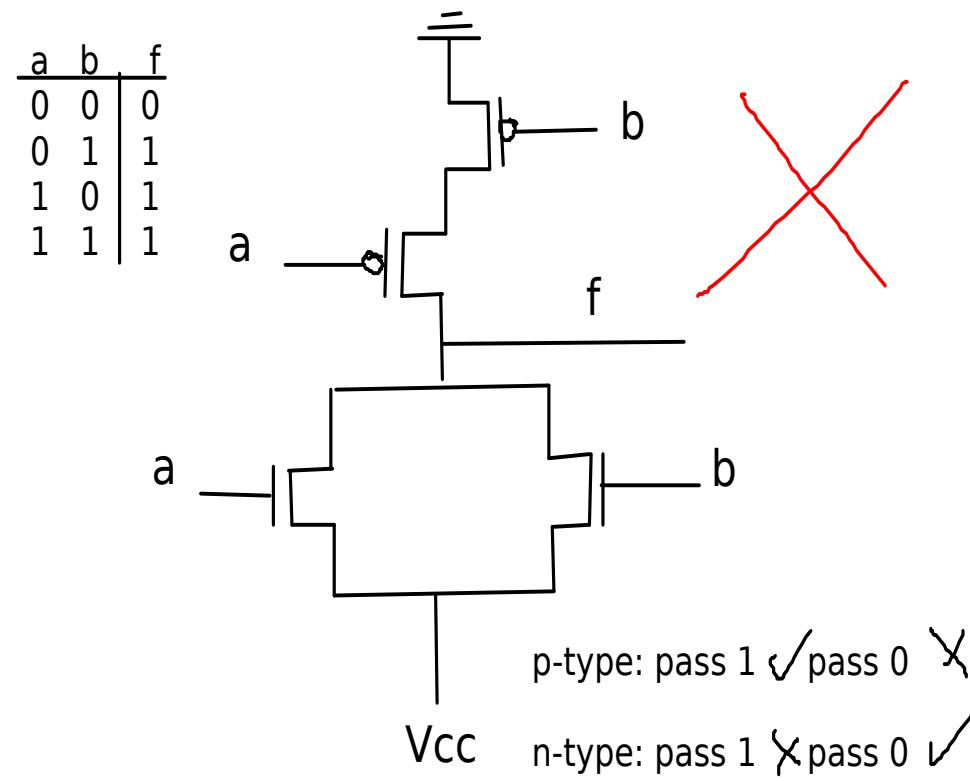


CMOS Or Gate cont.

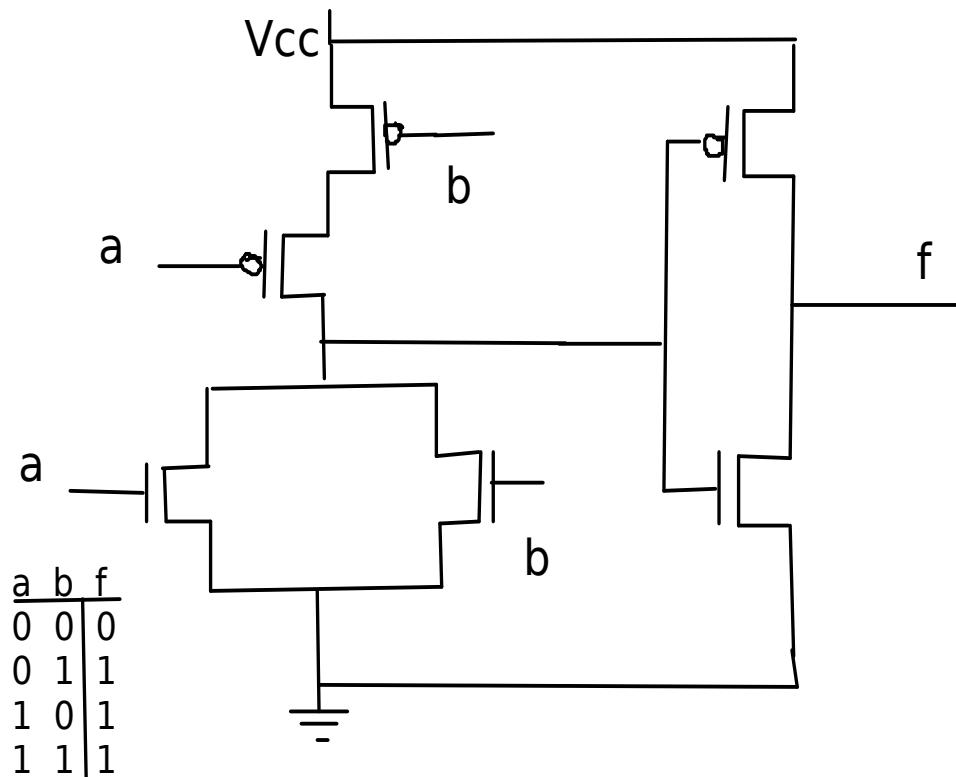


CMOS Nand Gate

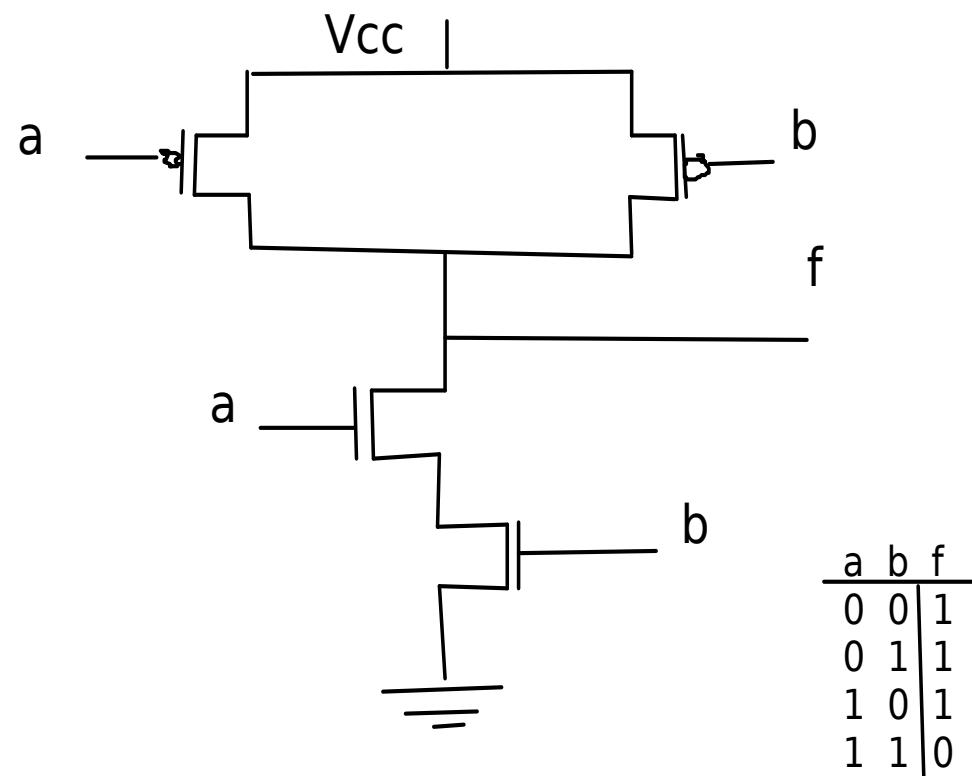

CMOS Transmission Gate

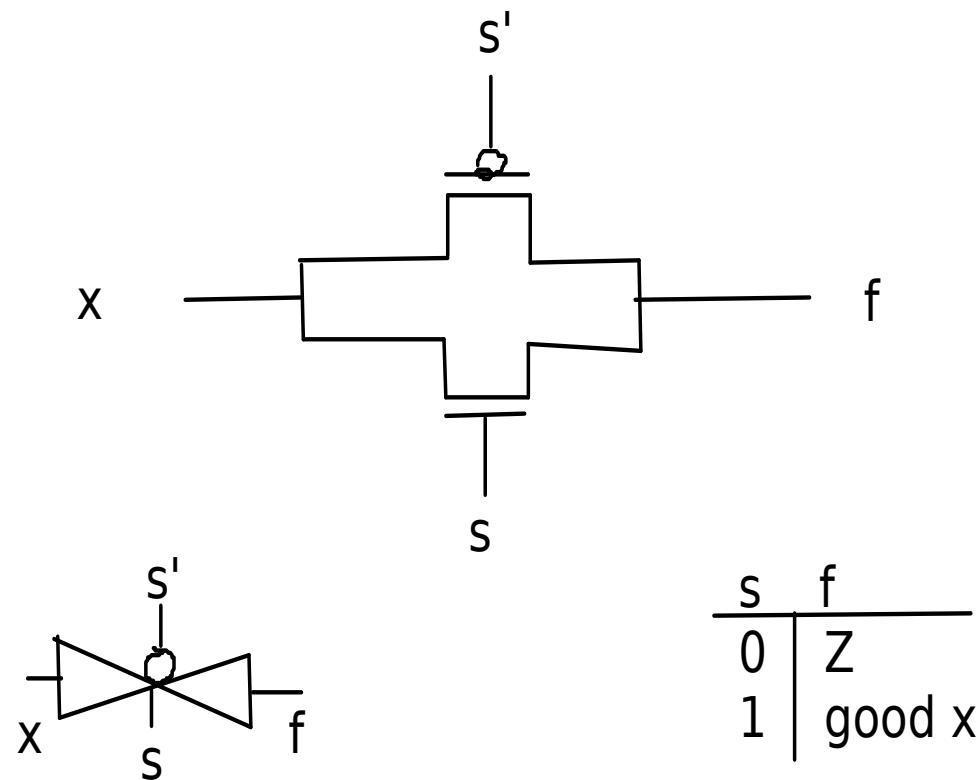

CMOS Xor Gate

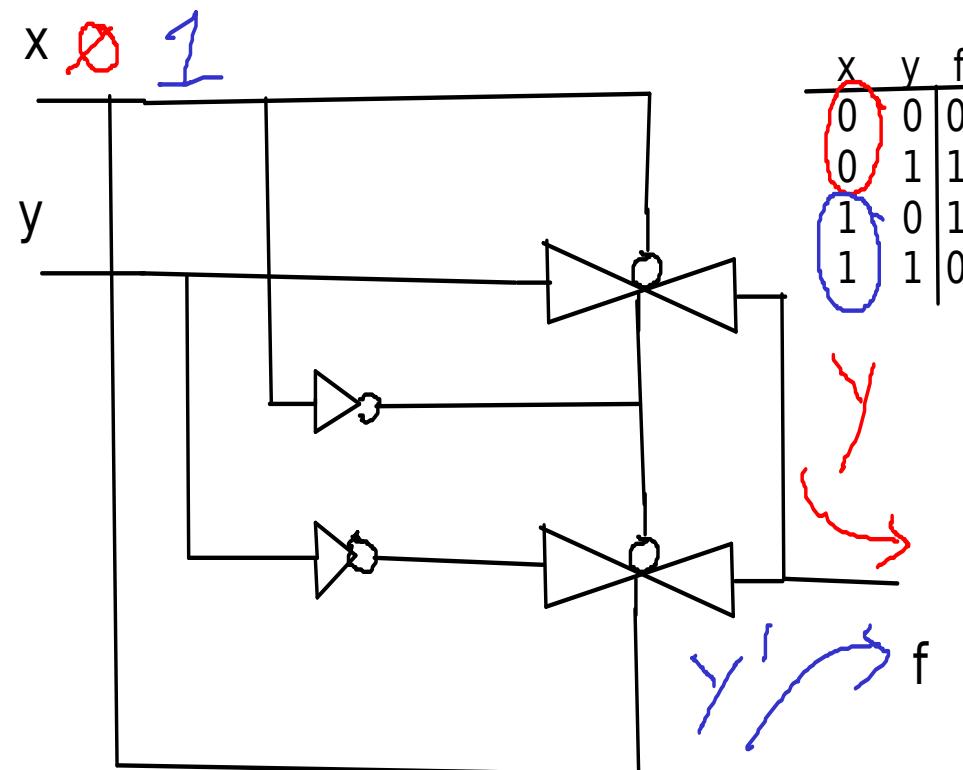

CMOS Gate Transistor Cost

- inverter
 - 2 transistors
- nand, nor
 - 4 transistors each
- and, or
 - 6 transistors each
- transmission
 - 2 transistors
- xor
 - 8 transistors (2 inverters, 2 transmission gates)
 - 22 transistors (2 inverters, 2 and gates, 1 or gate)