

# Computer Science CSCI 355

## Digital Logic and Computer Organization

*Dr. Peter Walsh*

*Department of Computer Science*

*Vancouver Island University*

*[peter.walsh@viu.ca](mailto:peter.walsh@viu.ca)*


## Bigger Building Blocks

- MSI

- Decoders
- Encoders
- Multiplexors
- Demultiplexors


# Decoders

○ e.g. 2 x 4 decoder

 

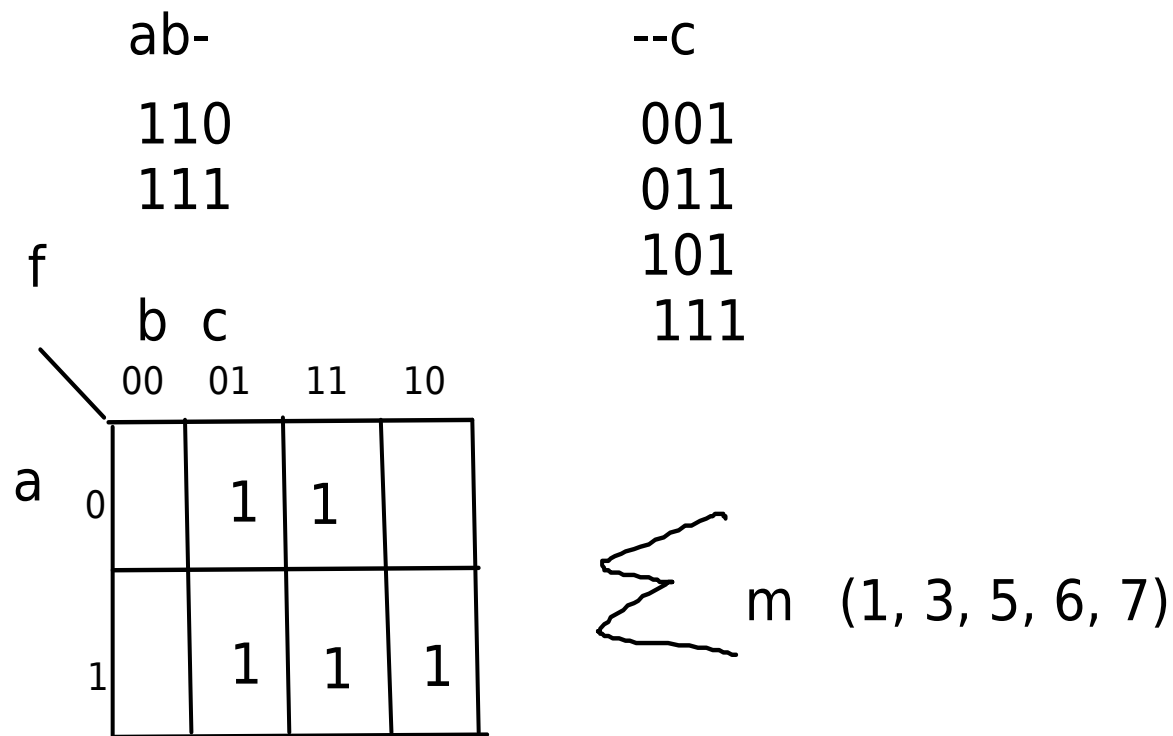
## Decoders cont.

- e.g. Implement  $f(a, b, c) = ab + c$  using 3 x 8 decoder




## Decoders cont.

○  $f = \sum m(1, 3, 5, 6, 7)$

 


# RAM/ROM (14 bit address - 8 bit data)

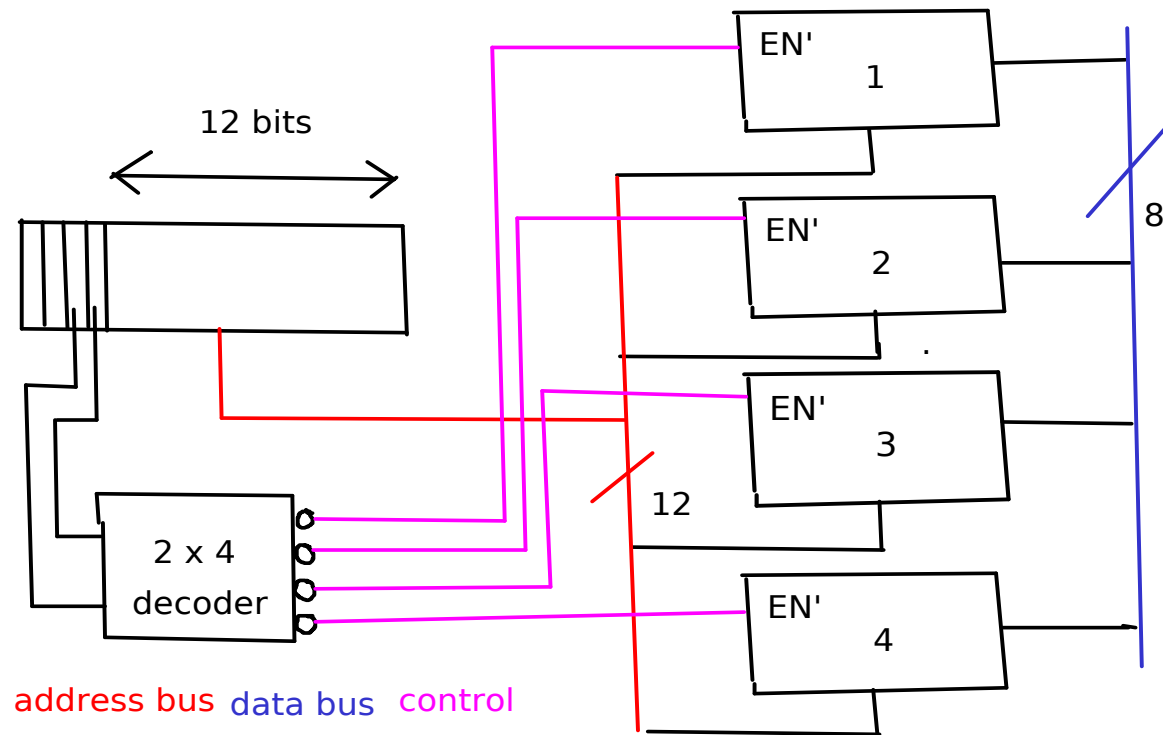
 
## Decoders cont.

- active high inputs
- active low outputs
- active low enable



# Encoder

D0	D1	D2	D3	x	y
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

0 1 2

$$x = D2 + D3$$

$$y = D1 + D3$$

x

	00	01	11	10
00	-	1	-	1
01	0	-	-	-
11	-	-	-	-
10	0	-	-	-

D0 D1/  
D2 D3

y

	00	01	11	10
00	-	1	-	0
01	1	-	-	-
11	-	-	-	-
10	0	-	-	-




# Priority Encoder

D0	D1	D2	D3	x	y	z
0	0	0	0	-	-	0
1	0	0	0	0	0	1
-	1	0	0	0	1	1
-	-	1	0	1	0	1
-	-	-	1	1	1	1

*Handwritten annotations:* Red circles around the '1 0' in the fourth row and the '1 2' in the fifth row. A red '2' is written to the right of the fourth row.


# Multiplexors

○ e.g. 4 to 1 multiplexor

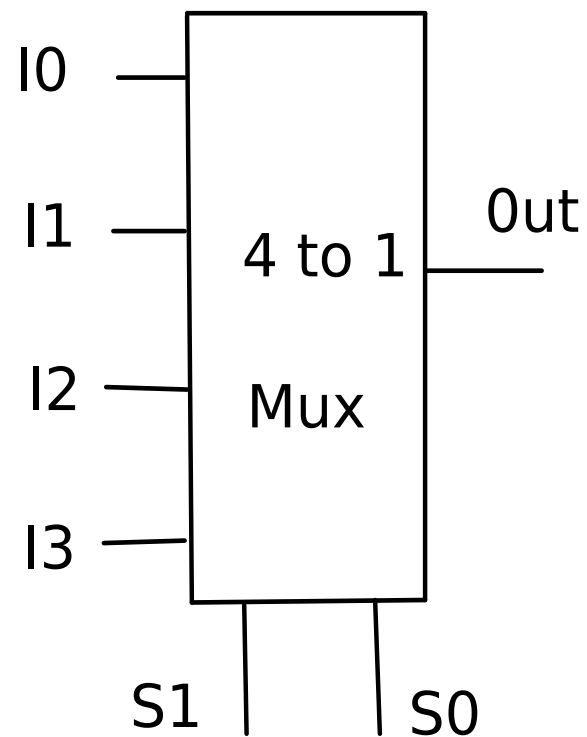


S1	S0	Out
0	0	I0
0	1	I1
1	0	I2
1	1	I3

# Multiplexors cont.

 

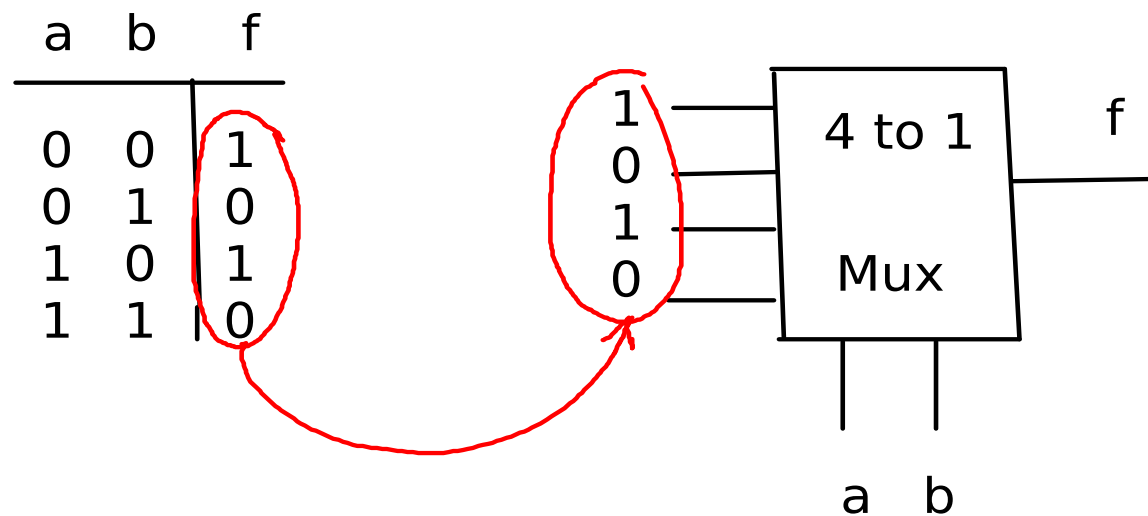
## Multiplexors cont.

- e.g. Implement  $f$  using 4 to 1 multiplexor


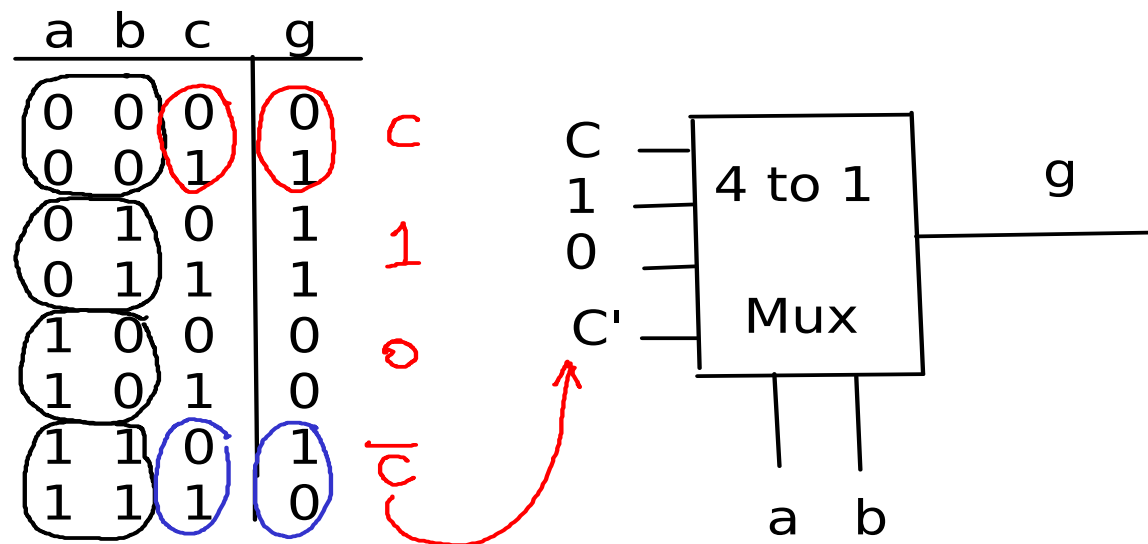
## Multiplexors cont.

- e.g. Implement  $g$  using 4 to 1 multiplexor




## Multiplexors cont.

- e.g. Implement  $z(a, b, c, d, e)$  using 3 4-to-1 multiplexors

			d e			
			I0	I1	I2	I3
a	b	c	00	01	10	11
0	0	0	0	0	0	1
0	0	1	0	1	1	1
0	1	0	0	1	1	1
0	1	1	1	1	1	1
1	0	0	0	1	1	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

1

# Multiplexors cont.

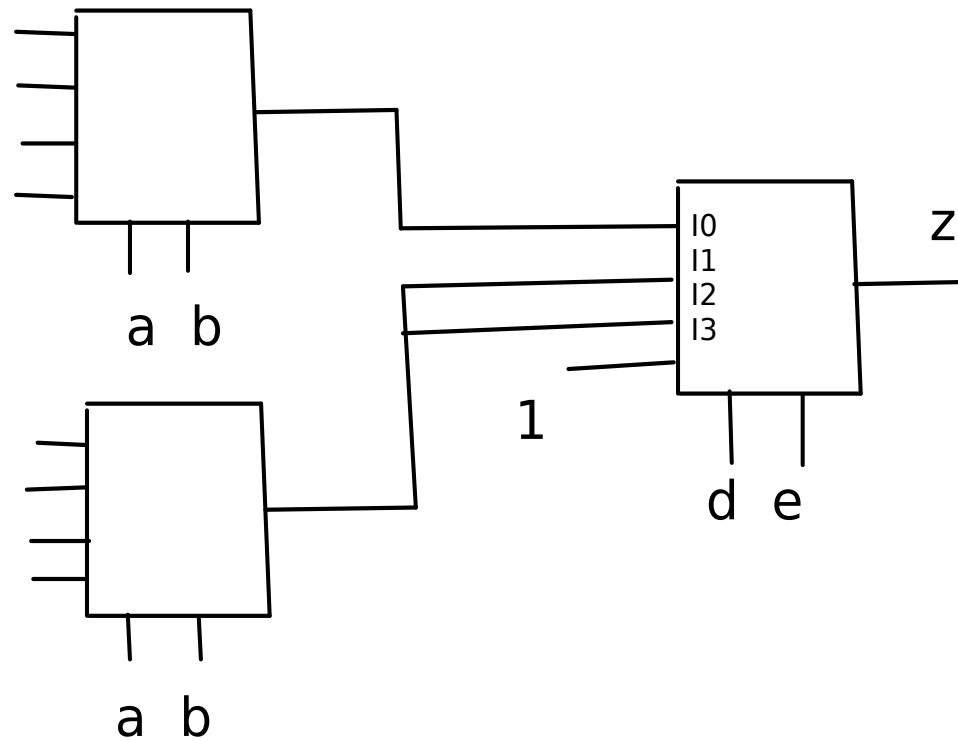

# Multiplexors cont.

			d e			
			I0	I1	I2	I3
a	b	c	00	01	10	11
0	0	0	0	0	0	1
0	0	1	0	1	1	1
0	1	0	0	1	1	1
0	1	1	1	1	1	1
1	0	0	0	1	1	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1



# Multiplexors cont.

